



**Habib University**  
**Electrical Engineering Department**  
**Dhanani School of Science & Engineering**

Course	EE/CE – 211 – Basic Electronics
Semester	Spring 2024
Section	Section L2
Exam	Quiz – 4
Instructor	Dr. Ahmad Usman
Total Marks	10


**Question – 1 (CLO 2, Points: 1.5 + 5 + 1.5 + 2)**

Consider an npn transistor-based amplifier circuit, biased in common emitter configuration, and having the following parameters:  $V_{CC} = 2.5 \text{ V}$ ,  $I_S = 3 \times 10^{-16} \text{ A}$ ,  $R_C = 100 \Omega$ ,  $V_{BE} = 800 \text{ mV}$ ,  $\beta = 100$ . The amplifier is having a microphone attached at the input (i.e., base terminal) and the amplified output is observed at the collector terminal.

- Draw the circuit diagram of the amplifier circuit clearly representing each of the important components.
- Calculate  $I_C$ ,  $I_B$ ,  $I_E$ ,  $V_{CE}$ ,  $g_m$ , and  $r_\pi$ .
- Draw the equivalent small-signal model of the transistor. Assume no-early effect.
- Assuming a 2 mV of input signal at the microphone, calculate the amplified signal voltage at the output.

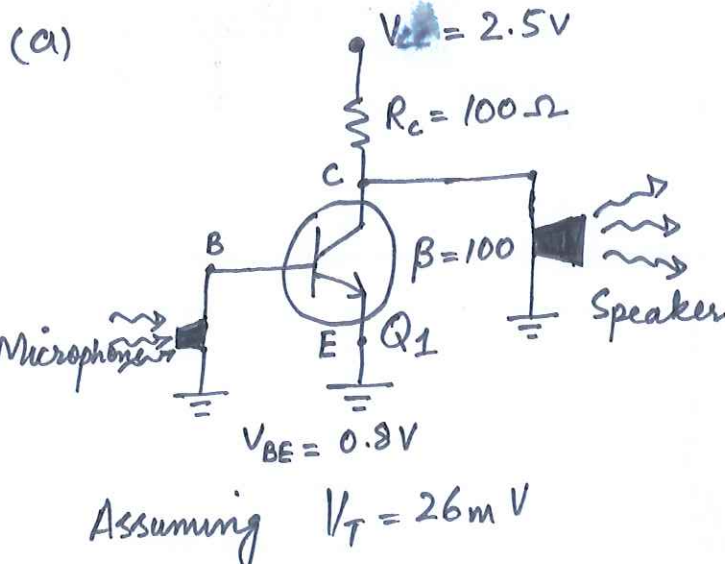**\*Bonus: (Points: 3)**

Does the input signal qualifies as a small-signal? Calculate the voltage swing at the output with respect to the Q-point of the circuit. Does the transistor remain in forward active region of operation or not? Use your calculations to justify your answer.



(b)  $I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$

$I_C = 6.998 \text{ mA}$

$I_C = \beta I_B$

$I_B = 69.987 \mu \text{ A}$

$I_E = I_C + I_B$

$I_E = 6.9871 \text{ mA}$

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = 1.8082 \text{ V}$$


$$g_m = \frac{I_C}{V_T}$$

$$g_m = 0.26607 \Omega^{-1}$$

$$r_\pi = \beta / g_m$$

$$r_\pi = 375.831 \Omega$$

(C) Small-Signal Model

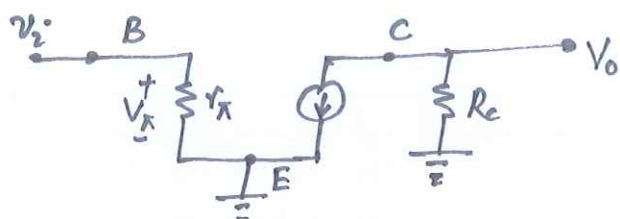

$$(d) \Delta i_c = g_m \Delta V_{BE}$$

$$\Delta V_{BE} = v_{in} = 2 \text{ mV}$$

$$\Delta i_c = 0.266 \times 2 \text{ m} = 0.532 \text{ mA}$$

$$\Delta v_o = (\Delta i_c) R_C = 53.2 \text{ mV}$$



$$A_v = \frac{v_o}{v_{in}} = \frac{53.2 \text{ m}}{2 \text{ m}} = 26.6$$

X ————— X

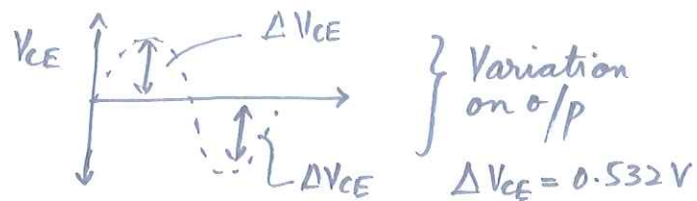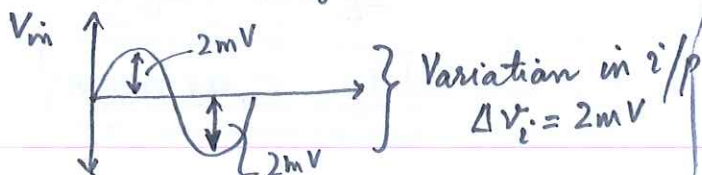**BONUS**

$$\frac{v_{in}}{V_{CC}} = \frac{2 \text{ m}}{2.5} \times 100 = 0.08\% < 1\%$$

The input signal is less than 1% of  $V_{CC}$ . It qualifies as a small-signal.



This cause  $V_{CE,Q}$  to vary.

$$V_{CE,Q(\max)} = 1.8082 + 0.532 = 2.3402 \text{ V}$$

$$V_{CE,Q(\min)} = 1.8082 - 0.532 = 1.2762 \text{ V}$$

For  $V_{CE(\max)}$

$$V_{BE} = 0.8 \text{ V (Forward Bias)}$$

$$V_{CB} = 1.0682 \text{ V (Reverse Bias)}$$

→ Transistor stays in "Forward Active Region".

For  $V_{CE(\min)}$

$$V_{BE} = 0.8 \text{ V (Forward Bias)}$$

$$V_{CB} = 0.9562 \text{ V (Reverse Bias)}$$

→ Transistor stays in "Forward Active Region".

